

# Impact of Technology Scaling on Low Noise Front End Circuits


Paul O'Connor, Brookhaven National Laboratory

Snowmass 2001

July 9 2001
 
# Charge preamplifier/shaper as detector front end

- Low noise is critical for many experiments
  - *Ageing of gas detectors*
  - *Fast, inefficient scintillators*
  - *Thin semiconductors for tracking*
  - *Position determination by interpolation*
  - *Particle ID by  $dE/dx$*



- *Input: charge pulse from capacitive source*
- *Output: filtered voltage pulse*
- *System noise is dominated by the input transistor*

# Outline

- Low noise analog design in monolithic CMOS
  - *Preamplifier design*
  - *Shaping amplifier*
- Circuit examples
- MOS Scaling and CSA design
  - *Noise mechanisms in scaled devices*
  - *Optimum capacitive match to detector*
  - *Noise, dynamic range, and power vs. scaling length*
- Interconnect issues
  - *Detector-to-preamplifier*
  - *Front end-to-ADC*

# Low Noise Analog Design

# MOS Charge Amplifier Design

- Key parameters:

- $C_{det}$ ,  $I_{det}$ ,  $Q_{max}$

*(detector)*

- $Rate$ ,  $P_{diss}$

*(system)*

- $f_T$ ,  $K_F$ ,  $I_{in}$


*(technology)*

- Key design decisions

- $C_{gs}/C_{det}$


- *Reset system*

- *Weighting function*

 


# MOSFET Channel Thermal Noise


- Drain current and its fluctuation:

 

# MOSFET connected to detector

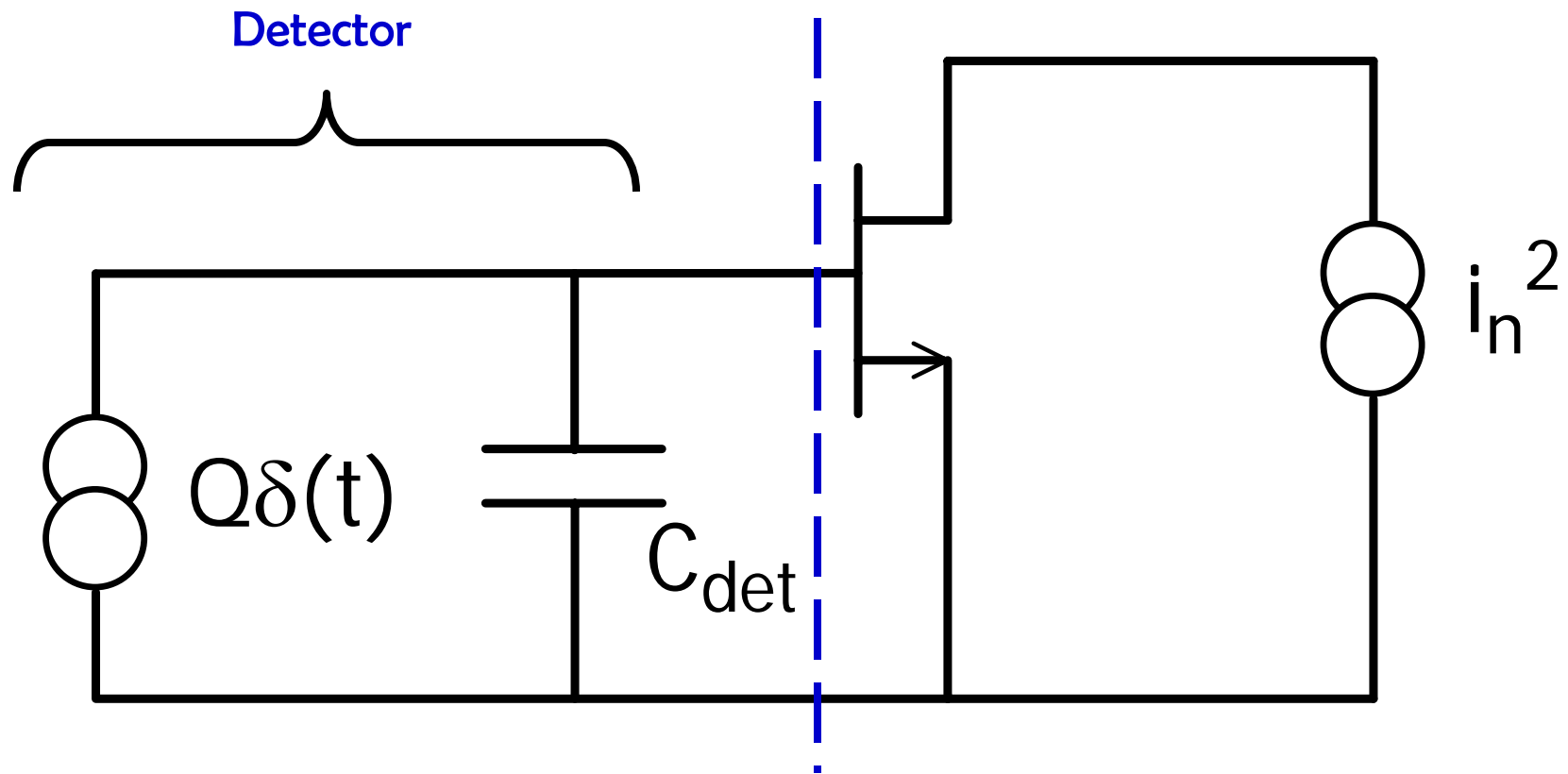


# Transform noise to input

 

$$e_n^2 = \frac{4kT\gamma}{g_m} + \frac{K_F}{C_{gs}f}$$



# Equivalent input noise charge

 

$$ENC^2 = \left( \frac{4kT}{g_m t_m} + \frac{K_F}{C_{gs}} \right) C_{in}^2$$

# Device sizing for minimum ENC

- Increasing MOS size decreases noise sources while increasing transistor contribution to  $C_{in}$

$$ENC^2 = \left( \frac{4kT}{g_m \cdot t_m} + \frac{K_F}{C_{gs}} \right) C_{in}^2$$

$$C_{in} = C_{gs} + C_{det}$$

=> optimum transistor size for series white and 1/f noise:

$$C_{gs,sw,opt} = \alpha_{sw} C_{det}$$

$$C_{gs,1/f,opt} = \alpha_{1/f} C_{det}$$

# Optimized ENC


- Transistor cutoff frequency  $g_m = C_{gs} \cdot \omega_T = C_{gs} / \tau_{el}$

$$ENC_{sw,opt} \approx \sqrt{kTC_{det}} \sqrt{\frac{\tau_{el}}{t_m}}$$
$$ENC_{1/f,opt} \approx \sqrt{K_F C_{det}}$$

- Key ingredients for low ENC:
  - *low*  $C_{det}$
  - *long*  $t_m$
  - *short*  $\tau_{el}$
  - *Low*  $K_F$
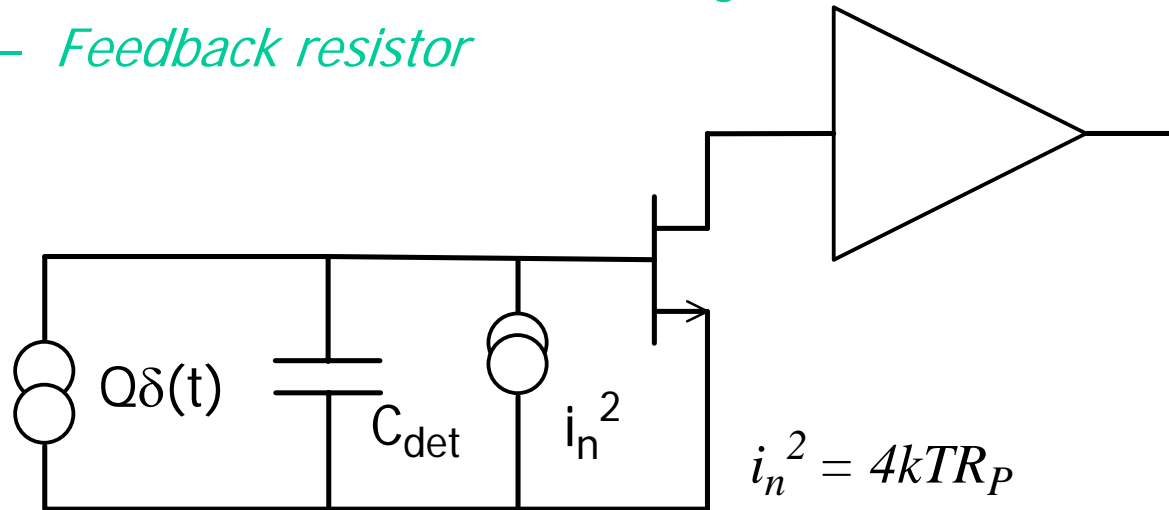
# Parallel noise


- From any noise current source connected to input:
  - *Detector biasing resistor*
  - *Shot noise of detector leakage current*
  - *Feedback resistor*



$$ENC_{par} = \sqrt{\frac{4kTt_m}{R_p}}$$

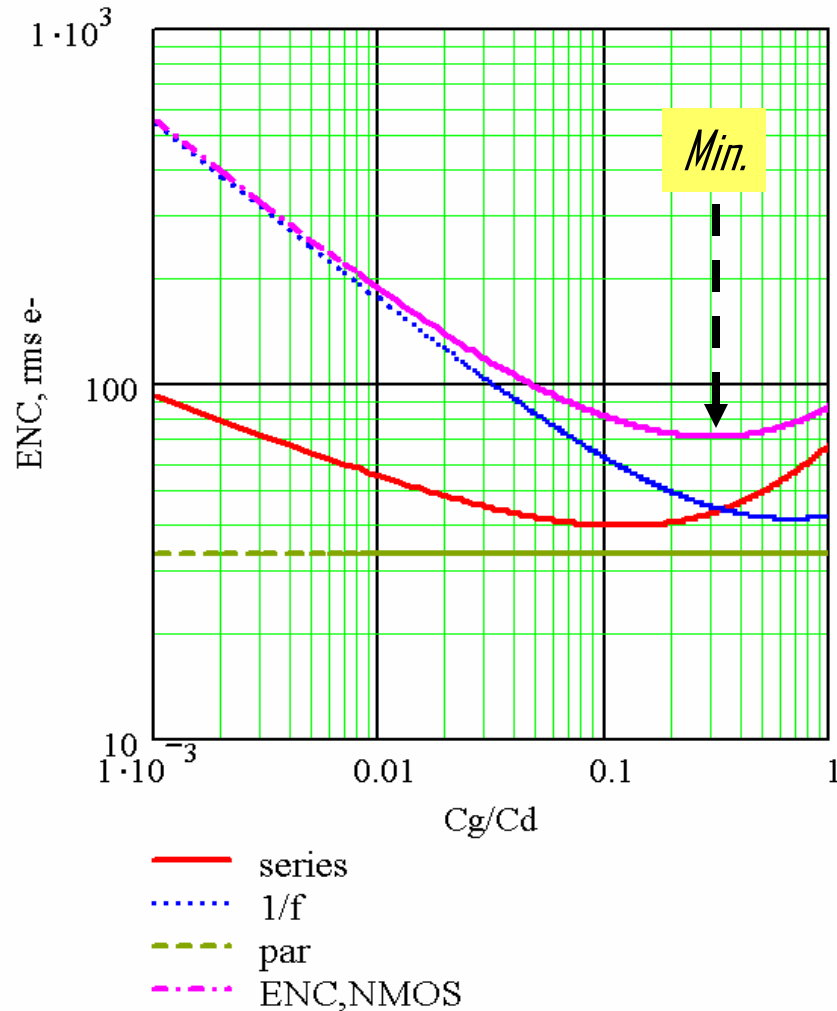
# Capacitive matching – composite noise

- $C_{det} = 3 \text{ pF}$
- $t_m = 1 \text{ } \mu\text{s}$
- $P_{diss} = 1 \text{ mW}$
- $I_{leak} = 100 \text{ pA}$
- Technology:  $0.35 \text{ } \mu\text{m}$  NMOS



 
# Basic Charge Amplifier


Configuration based on discrete/hybrid design



CMOS implementation

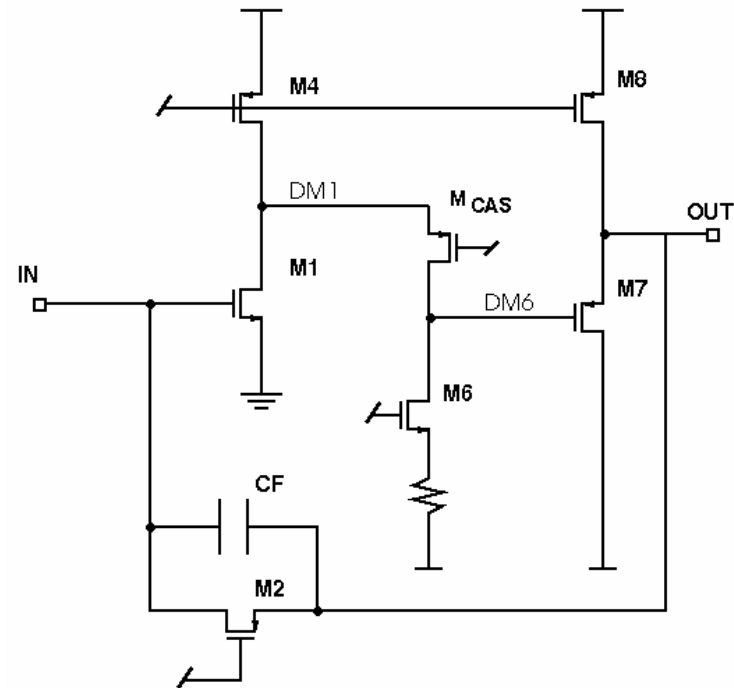


  
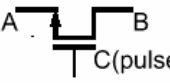
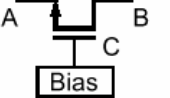
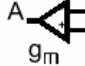

# Preamp Reset – Requirements



- all charge preamplifiers need DC feedback element to discharge  $C_F$
- usually, a resistor in the  $M\Omega - G\Omega$  range is used
- monolithic processes don't have high value resistors
- we need a circuit that behaves like a high resistor and is also
  - *insensitive to process, temperature, and supply variation*
  - *low capacitance*
  - *lowest possible noise*
  - *linear*


# Preamp Reset – Configurations



Feedback type	Circuit	$R_{eff} (I_{leak} = 0)$	Advantages/ Disadvantages
Physical resistor	A  B	$R$	+ simple - hard to make large R - parasitic C - doesn't adjust to $I_{leak}$
MOS switch	A  B C(pulse)	$\frac{1}{C_F \cdot f_{reset}}$	+ simple - dead time - switch noise
Triode MOS	A  B C Bias	$\frac{1}{\beta \cdot (V_{gs} - V_T)}$	+ compact + adjusts to $I_{leak}$ - nonlinear
Feedback $g_m$	A  B $g_m$ C (Vref)	$\frac{1}{g_m}$	+ adjusts to $I_{leak}$ - complex - excess noise - nonlinear
Attenuating current mirror	A  B $A_i \ll 1$	$\frac{R}{A_i}$	+ aux. output for PZC - doesn't adjust to $I_{leak}$




# Nonlinear Pole-zero Compensation

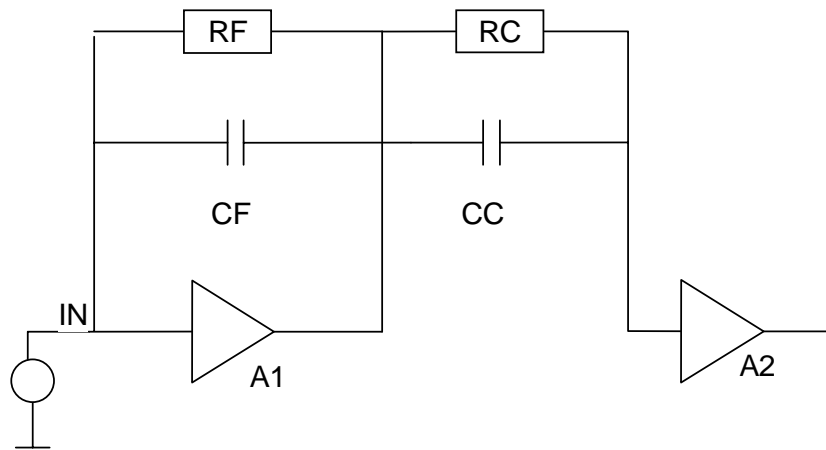

- Classical

 - $RF \cdot CF = RC \cdot CC$
- Zero created by  $RC, CC$  cancels pole formed by  $RF, CF$



- IC Version





- $CC = N \cdot CF$
- $(W/L)_{MC} = N \cdot (W/L)_{MF}$
- Zero created by  $MC, CC$  cancels pole formed by  $MF, CF$
- Rely on good matching characteristics of CMOS FETs and capacitors

G. Gramegna, P. O'Connor, P. Rehak, S. Hart, "CMOS preamplifier for low-capacitance detectors", NIM-A 390, May 1997, 241 – 250.

# Integrated Shaping Amplifiers


- Limits the bandwidth for noise
- Gives controlled pulse shape appropriate for rate
- Control baseline fluctuations
- Bring charge-to-voltage gain to its final value
- By its saturation characteristics, sets upper limit on  $Q_{in}$
- Feedback circuits give the most stable and precise shaping
  - *At the expense of power dissipation*
  - *Poor tolerance of passives limits accuracy of the poles and zeros*
- High-order shapers give the lowest noise for a given pulse width

## Filter topologies

 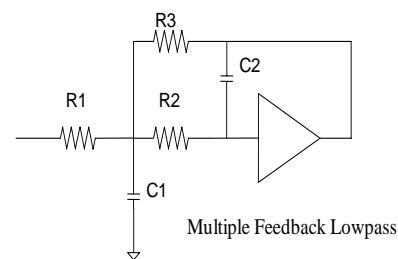  

# Complex pole approximation to Gaussian pulse

Shaper Pole Positions

 

---■--- Gaussian    ---■---    ▲ CR2RC6

**Dhkawa synthesis method** (Dhkawa, NIM 138 (1976) 85-92, "Direct Syntheses of the Gaussian Filter for Nuclear Pulse Amplifiers")

For given filter order, gives closest approx. to a true Gaussian


More symmetrical than CR-RC<sup>n</sup> filter of same order for same peaking time

Noise weighting functions:

$$I_{1,\text{complex}}/I_{1,\text{CR-RC}} = 1.18 \quad \text{series}$$


$$I_{2,\text{complex}}/I_{2,\text{CR-RC}} = 0.81 \quad \text{parallel}$$

# Complex shapers: advantages

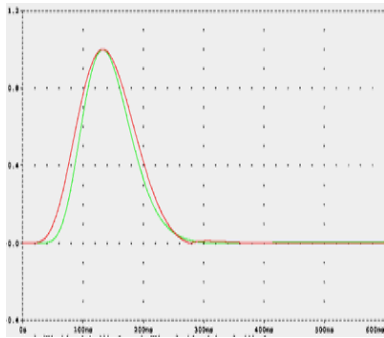


— 7th order complex  
— 12th order CR-RC<sup>n</sup>

Equal peaking times,  
equal 1% widths

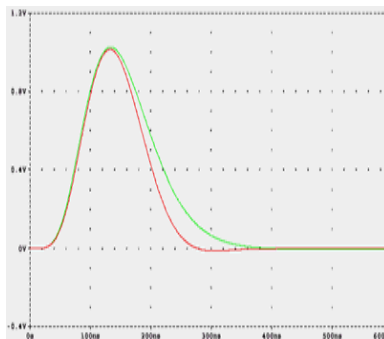

— 7th order complex  
— 7th order CR-RC<sup>n</sup>

Equal peaking times,  
equal order

 


— 7th order complex  
— 7th order CR-RC<sup>n</sup>

Equal 1% widths, equal  
order

# Examples

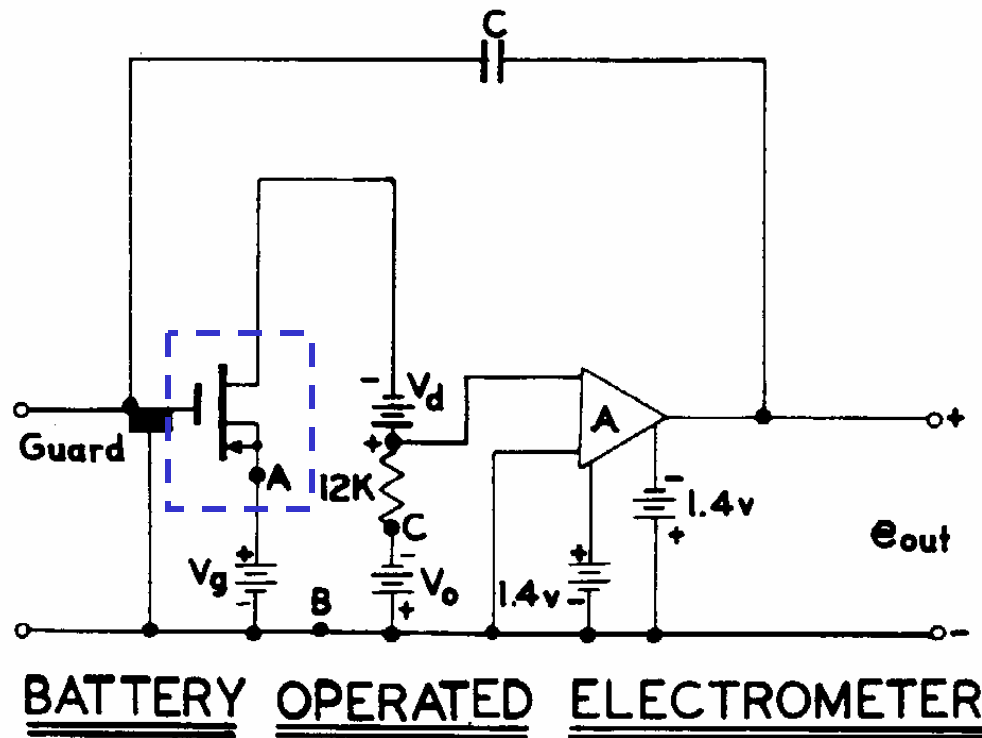
# Charge Amplifier based on Silicon MOSFET (1967)



V. Negro et al., "A Guarded Insulated Gate Field Effect Electrometer", IEEE Trans. Nucl. Sci. Feb. 1967, 135 – 142

J.B. McCaslin, "A Metal-Oxide-Semiconductor Electrometer Ionization Chamber", UCRL-11405 (1964)


# Spectroscopy amplifier (1989)

 

Technology	3.0 $\mu\text{m}$ CMOS
Power Supply	+/- 5V
Chip size	2.5 x 2.5 mm
Channels	1
$C_{det}$	300 - 1000 pF
Reset	external resistor
Shaping	CR-RC <sup>4</sup> , 1.6 $\mu\text{s}$
ENC	3800 + 4.1 e <sup>-</sup> /pF
Power dissipation	96 mW

Z. Chang, W. Sansen, *Low-Noise Wide-Band Amplifiers in Bipolar and CMOS Technologies*, Kluwer 1991 Ch. 5
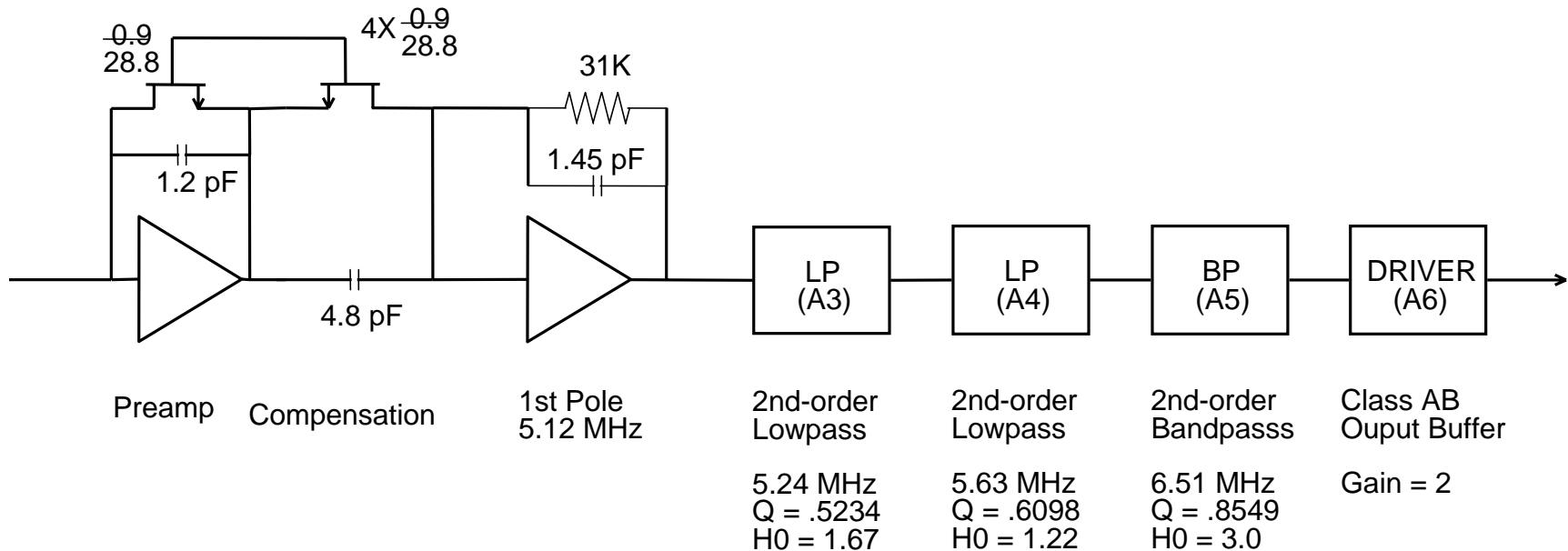
# Preamp-shaper for cathode strip chamber





- Detector: cathode strips of 0.5m MWPC with 50 pF  $C_{DET}$
- Charge interpolation to 1/100 of the strip pitch
- Fast (70 ns), 7<sup>th</sup> order bipolar shaping for charged particle tracking in high rate environment




  
# Preamp-shaper for cathode strip chamber


Pulse Shape simulated (solid red line) and measured (blue dotted line)



 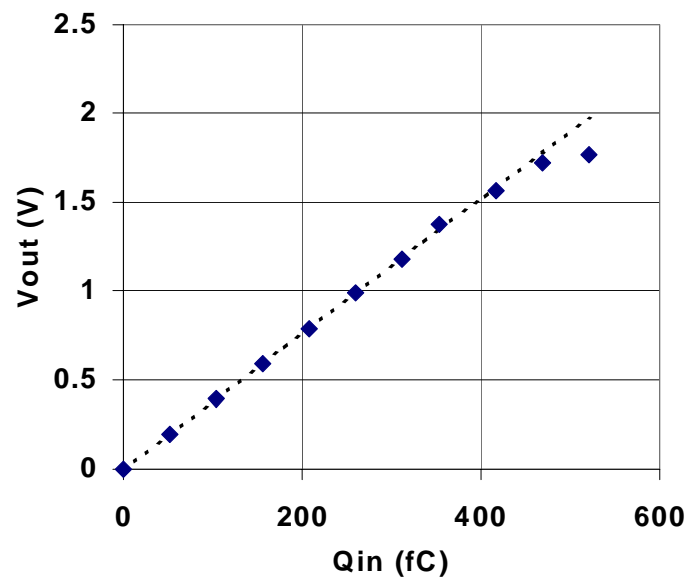Simulated:  $\times$   
Measured:  $\circ$



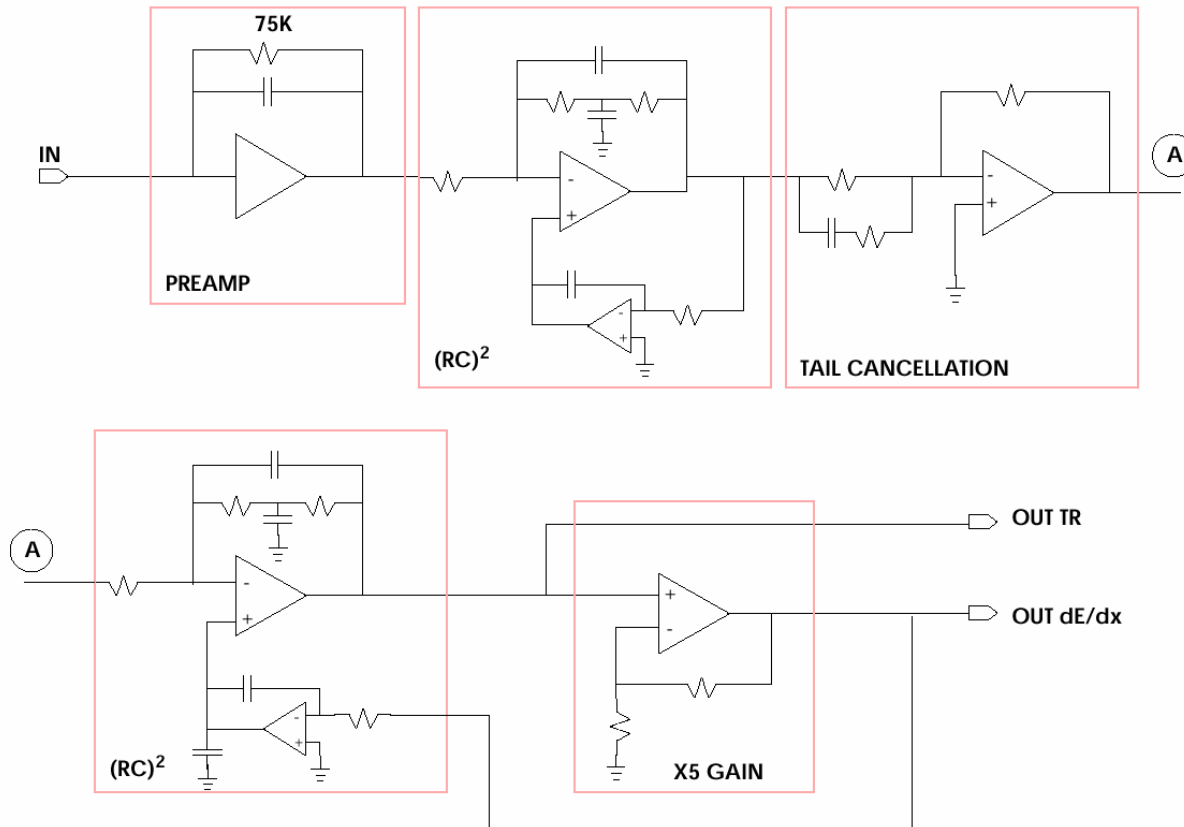
# Time Expansion Chamber & Transition Radiation Detector Preamp/Shaper




- 1m MWPC with 20 pF  $C_{DET}$
- Fast (70 ns) shaping for charged particle tracking
- Dual gain outputs for measurement of dE/dx and Transition Radiation

# TEC-TRD Preamp/Shaper


## Block Diagram

 

## Die Layout

 


## X-ray Response

 


A. Kandasamy, E. O'Brien, P. O'Connor, W. VonAchen, "A monolithic preamplifier-shaper for measurement of energy loss and transition radiation" IEEE Trans. Nucl. Sci. 46(3), June 1999, 150-155

# Drift Detector Preamplifier

HP 1.2um version

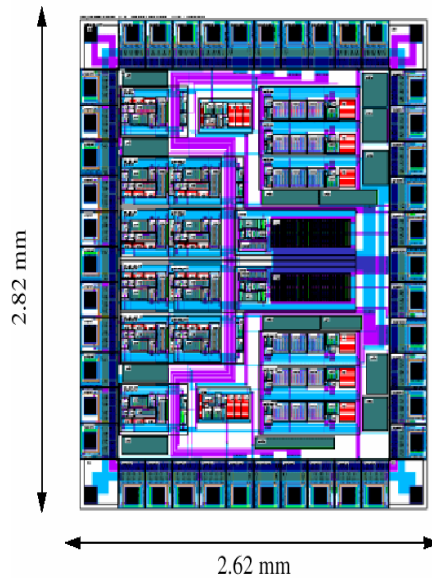

AMS 1.2um version

 


Requirements for 100 eV resolution with a 0.2 pF detector at 1 - 5  $\mu$ s shaping time:


- $I_{leak} < 10$  pA
- $R_F > 3$  G $\Omega$
- $g_m > 0.4$  mS
- $K_F < 1.8 \times 10^{-25}$  J

- Used with ultra-low capacitance silicon drift detector,  $C_{det} < 0.3$  pF
- Preamp only, used with external shaper
- Purpose: explore lowest noise possible with CMOS
- Reset system: MOS transistor with special bias circuit to achieve stable,  $> 100$  G $\Omega$  equivalent resistance

Detector

 
 
# Drift detector preamplifier – simplified schematic




hnl



Preamplifier

Bias Circuit

# Drift Detector & CMOS Preamplifier

 

# Drift detector preamplifier – results


 
 


- Spectra of  $^{241}\text{Am}$  and  $^{55}\text{Fe}$  taken with 5mm  $\Phi$  Si drift detector and CMOS X-ray preamplifier. Detector and circuit cooled to  $-75\text{ C}$ .
- External 2.4  $\mu\text{s}$  shaping.
- ENC = 13  $e^-$  rms.
- Noise without detector: 9  $e^-$

P. O'Connor et.al., "Ultra Low Noise CMOS Preamplifier-shaper for X-ray Spectroscopy", NIM A409 (1998), 315-321



# SVT 240-channel Multi-Chip Module

  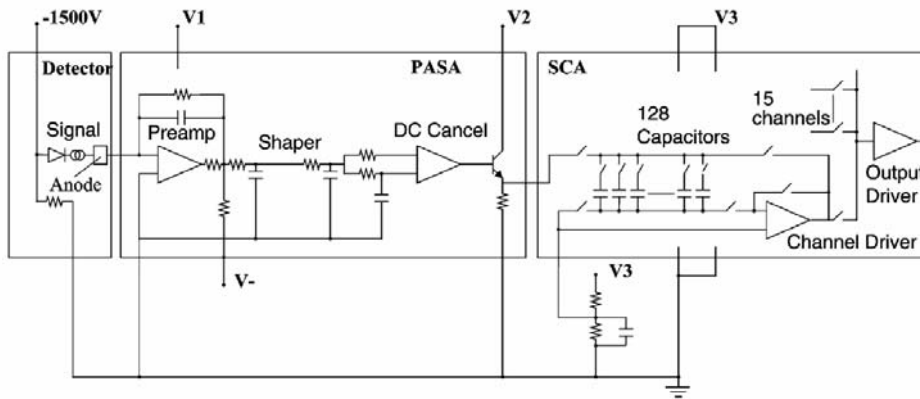

D. Lynn et al., "A 240 channel thick film multi-chip module for readout of silicon drift detectors", NIM A439 (2000), 418 - 426




# BNL Preamp/Shaper ICs, 1995 - 2001

PROJECT	Hi-res. Spectroscopy	RHIC - PHENIX	RHIC - STAR	LHC - ATLAS	Industry Partnership	NSLS - HIRAX	Units
DETECTOR	Si drift	Time Expansion Chamber	Silicon Vertex Tracker	Cathode Strip Chamber	CdZnTe gamma ray detector	Si Pixel	
Function	Preamp	Preamp/Shaper	Preamp/Shaper	Preamp/Shaper	Preamp/Shaper	Preamp/Shaper/Counter	
C <sub>DET</sub>	0.3	30	3	50	3	1.5	pF
Peaking Time	2400	70	50	70	600:1200:2000:4000	500:1000:2000:4000	ns
Gain	10	2.4:12 - 10/25	40:70:90	4	30:50:100:200	750:1500	mV/fC
Power	10	30	3.8	33	18	7	mW/channel
ENC	10	1250	400	2000	100	24	rms electrons
Dynamic Range	1250	4600	700	1900	5600		
Technology	CMOS 1.2 um	CMOS 1.2 um	Bipolar 4 GHz	CMOS 0.5 um	CMOS 0.5 um	CMOS 0.35 um	
Input Transistor	PMOS 150/1.2 um	NMOS 4200/1.2 um	NPN 10 uA	NMOS 5000/0.6 um	NMOS 200/0.6 um	PMOS 400/0.4 um	
Reset Scheme	Compensated PMOS, > 1GΩ	Polysilicon, 75 kΩ	Nwell, 250 kΩ	Compensated NMOS, 30 MΩ	Compensated PMOS	Compensated NMOS	
No. Channels	6	8	16	24	16	32	
Die Size	7.3	15	8	20	19	16	mm <sup>2</sup>


# Practical amplifier considerations

- Preamplifier reset
- High order filters
- Programmable pulse parameters
- Circuit robustness:
  - Self-biasing
  - Low-swing, differential I/O
  - Circuits tolerant to variations in
    - Temperature
    - Process
    - Power supply
    - DC leakage current
    - Loading


Pulse vs. Temperature

 


Gain variation

 

Pulse vs.  $I_{leak}$

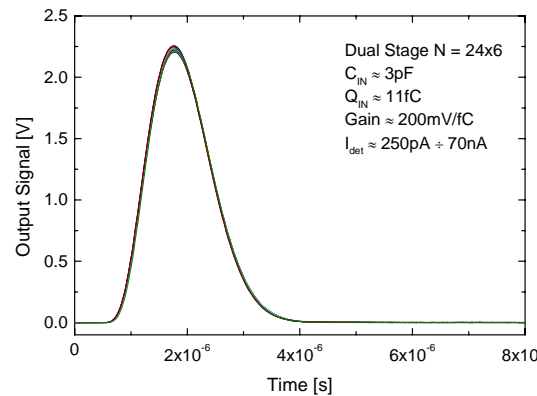

Peaking time variation

 

Baseline	< 0.3mV	< 30mV	< 0.1% $\Delta T$	< 8mV	-	$\Delta t_{peak} \sim 100ps$
Gain	< 0.1%	< 0.1%	< 0.1% $\Delta T$	< 0.1%	< 0.1%	start-walk on time
	leak	ripple	Temperature	(of) bias	nic	base


# **MOS Scaling and Charge Amplifier Design**

# Scaling issues

- Fundamental device noise mechanisms
  - *Hot electron effects*
  - *New process steps effect on 1/f noise*
  - *Gate tunnelling current*
- Change of the current-voltage characteristics
  - *Increase of weak inversion current*
  - *Mobility decrease*
  - *Velocity saturation*
  - *Drain conductance (device intrinsic DC gain)*
- Power supply scaling


 
# Series white noise

- Parameter  $\gamma = g_m * R_n$
- Some models predict  $\gamma \gg 1$  for short channel devices
- At moderate inversion and low  $V_{DS}$ ,  $\gamma$  remains in the range  $0.8 < \gamma < 1.4$
- Shallow junctions increase S/D series resistance => noise



 
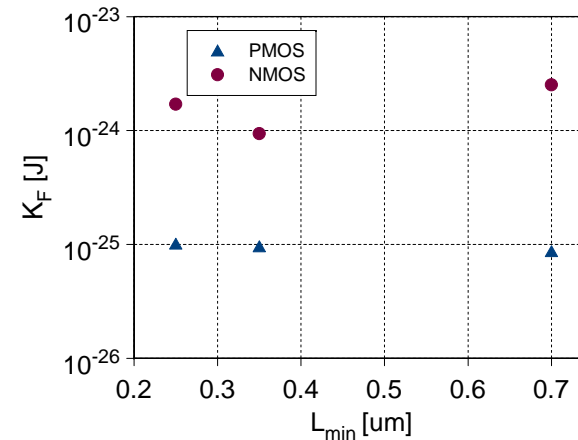
# 1/f noise in submicron CMOS

- Processes with n+/p+ poly gates and retrograde wells create surface-channel PMOS – PMOS 1/f noise to become more like NMOS?
- Shallow junctions required for scaled processes limit the thermal budget – hence gate process will have reduced post-oxidation anneal and higher trap density, higher 1/f
- For ultrathin gates new dielectrics with higher trap densities will be used (nitrided, halogenated, H2 annealed)



  
# 1/f noise and hot carrier stress

- Hot carrier stress generates new oxide/interface traps.
- 1/f noise more sensitive than change in static parameters:
  - $\Delta g_m$  -10%
  - $\Delta(1/f)$  +400%
- Worse for shorter channel lengths
- A device engineered for "acceptable" degradation of  $V_{th}$  and  $g_m$  may show unacceptable increase in 1/f noise over the same period.
- The operating point of the device will determine the stability of the long-term 1/f noise


 
# Gate tunneling current

- Gate current expected to increase 100 – 200 x per generation below 0.18  $\mu\text{m}$
- $J_{\text{ox}} \sim 100 \text{ A/cm}^2$  projected for  $L_{\text{min}} = 0.1 \mu\text{m}$  generation with nitrided  $\text{SiO}_2$
- Considered tolerable for digital circuits (total gate area per chip  $\sim 0.1 \text{ cm}^2$ )
- Typical CSA input FET would have  $I_G \sim 1 - 10 \mu\text{A}$ ;  $\text{ENCp} \sim 2000 - 7000$  rms e- at 1  $\mu\text{sec}$




$\text{SiO}_2$  gate leakage current (Lo et al., Electron Dev. Letters 1997)



 
# Departure from square-law characteristics

- Submicron devices are less often operated in strong inversion, square-law region.
- Influences behavior of series white thermal noise
- Square-law devices have minimum series noise when  $C_{gs} = C_{det} / 3$
- For other regions of operation, minimum noise can be for larger or smaller values of  $C_{gs}$


 
# Generalized capacitive matching condition

- Drain current = constant
- Ratio of  $C_{gs}$  to  $C_{det}$  determined by  $C_{det}/I_D$ :






$C_{det}/I_D$ Ratio	Region of operation	Optimum capacitive match
$\frac{C_{det}}{I_D} < \frac{6\mu}{v_{sat}^2}$	Velocity saturated	$C_{gs} = C_{det}$
$\frac{6L^2}{\mu(nkT/q)^2} < \frac{C_{det}}{I_D} < \frac{6\mu}{v_{sat}^2}$	Strong-inversion square-law	$C_{gs} = C_{det} / 3$
$\frac{C_{det}}{I_D} > \frac{6L^2}{\mu(nkT/q)^2}$	Weak inversion boundary	$C_{gs} = \frac{2L^2 I_D}{C_{det} (nkT/q)^2}$

P. O'Connor, G. De Geronimo, "Prospects for Charge Sensitive Amplifiers in Scaled CMOS", NIM-A accepted for publication
   
# Capacitive match vs. scaling – mixed white, 1/f and parallel noise

- $C_{det} = 3 \text{ pF}$ ,  $t_m = 1 \text{ } \mu\text{s}$ ,  $P_{diss} = 1 \text{ mW}$ ,  $I_{leak} = 100 \text{ pA}$




# Noise vs. scaling for mixed white, 1/f, and parallel noise


4 detector scenarios for scaling study

System	$C_{det}$	$t_{ce}$	P	$I_{leak}$	Detector	Typical Application
a	30	75	10	.001	Wire Chamber	Tracking, Imaging
b	15	25	0.2	10	Si Strip	Tracking
c	0.3	25	0.02	1	Si Pixel	Tracking
d	3	2500 – 500*	10	0.01	Semiconductor	Spectroscopy
UNITS	pF	ns	mW	nA	-	-

Noise vs. scaling

 

Optimum gate width vs. scaling

 


# Noise and Power vs. Scaling

4 detector scenarios for scaling study

System	$C_{det}$	$t_e$	P	$I_{leak}$	Detector	Typical Application
a	30	75	10	.001	Wire Chamber	Tracking, Imaging
b	15	25	0.2	10	Si Strip	Tracking
c	0.3	25	0.02	1	Si Pixel	Tracking
d	3	2500 – 500*	10	0.01	Semiconductor	Spectroscopy
UNITS	pF	ns	mW	nA	-	-


Noise vs. scaling

(power held constant)

 


Power vs. scaling

(noise held constant)

 


# Dynamic Range vs. scaling

 

**Interconnect**

# Cost of Interconnect


 







# Interconnect issues in monolithic front ends

- Detector – preamplifier
  - *Lowest possible capacitance*
  - *Maintain small form factor*
  - *Ease of assembly*
- Front end – ADC
  - *Efficient use of expensive “analog” interconnect*




# TEC Front-End Card

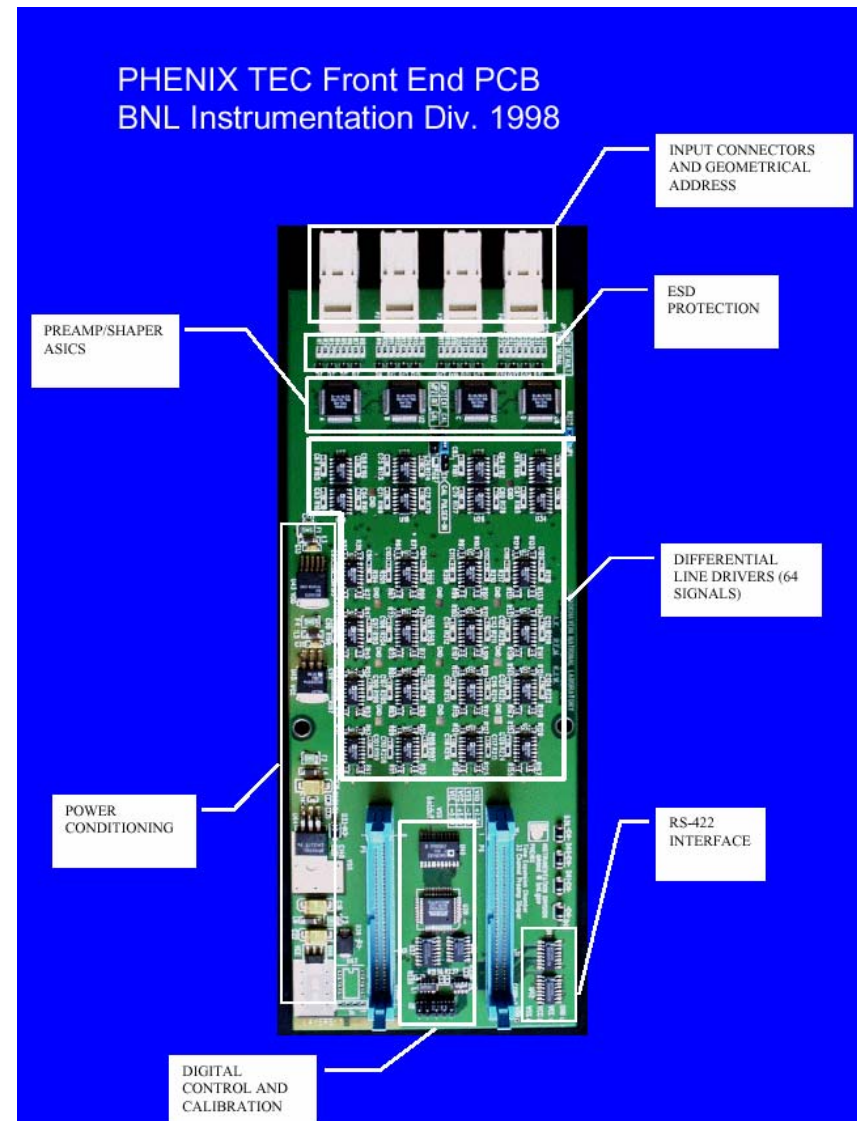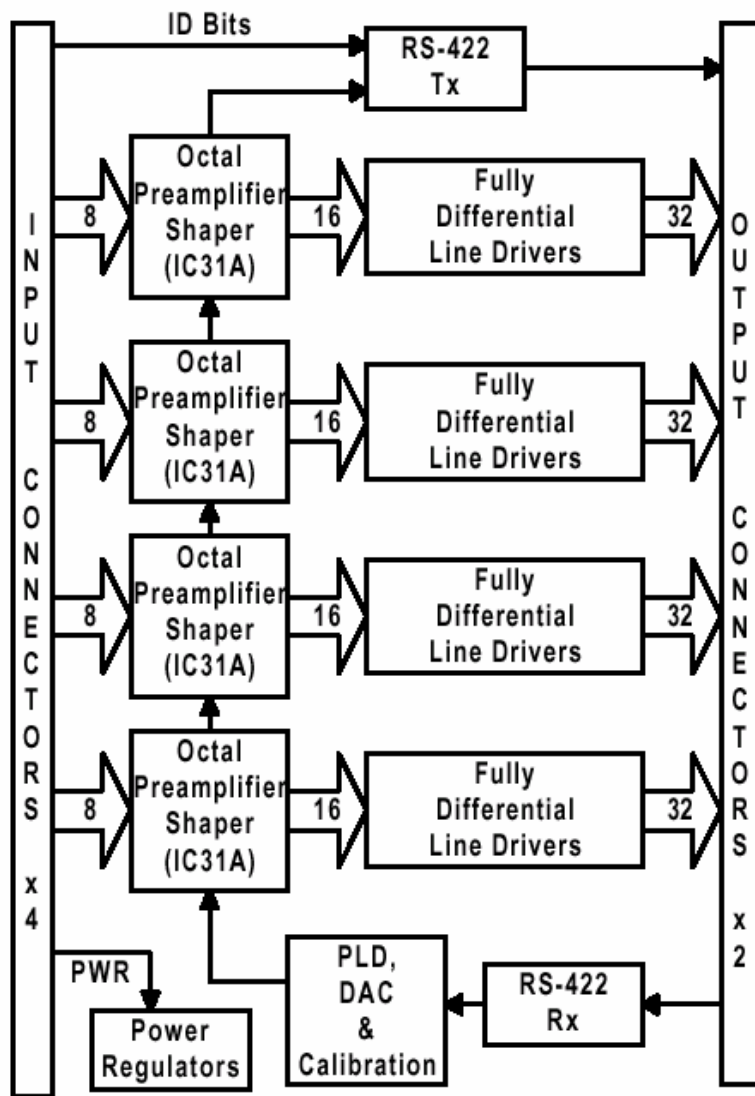

# Make the chip a part of the detector

   

# Make the detector part of the chip

   


# What goes between the preamp/shaper and the ADC?


- Experimental needs differ
  - *number of channels*
  - *occupancy*
  - *rate*
  - *trigger*
- Usually, its too expensive to put an ADC per channel
- Anyway the ADC would usually not be doing anything useful
  - *Occupancy < 100%, so no events most of the time in most channels*
- What is the most efficient way to use the ADC(s)?

# Analog Sampling and Multiplexing

Track-and-hold  
(triggered systems)


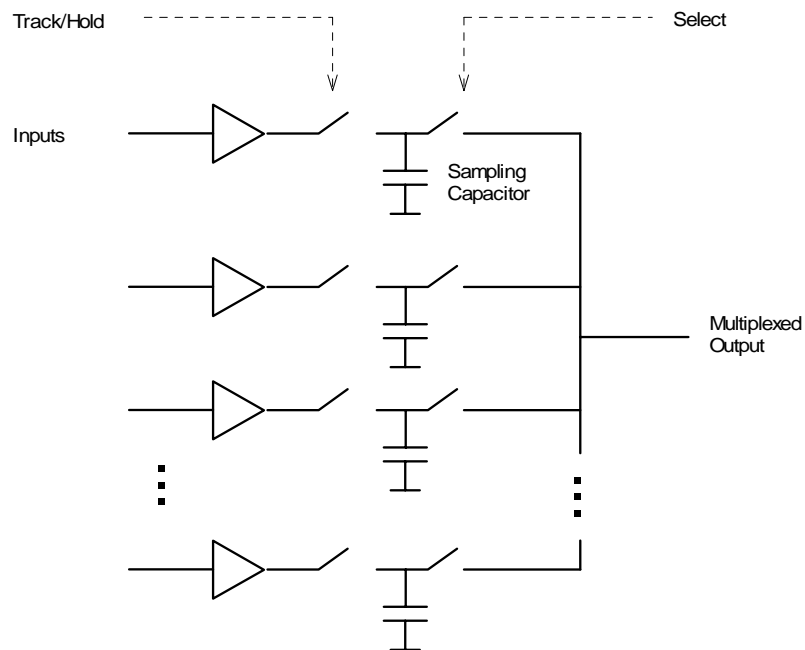


Analog memory  
(non-triggered)

 

  
# New Peak Detector and Derandomizer

- Self-triggered
- Self-sparsifying
- New 2-phase configuration allows rail-to-rail operation, eliminates offsets
  - *absolute accuracy ~ 0.2%*
  - *to within 300 mV of rails*
- Two or more peak detectors in parallel can be used to derandomize events
  - *If a second pulse arrives before the readout of the first pulse in Pd-a, it is detected and stored on Pd-b.*




# First experimental results

Accuracy of single PD

 

 PD/D response to random pulse train ( $^{241}\text{Am}$  on CZT)



G. DeGeronimo, P. O'Connor, A. Kandasamy, "Analog Peak Detect and Hold Circuits Part 2: The Two-Phase Offset-Free and Derandomizing Configurations", NIM-A submitted for publication



# Conclusions

- Today's CMOS technology can be used to make low noise front ends whose performance is nearly as good as the best discrete units
- In the future, increasing device cutoff frequency and gate oxide quality will help improve noise **BUT**
  - *Potentially serious increases in 1/f noise and gate current may accompany new process sequences*
  - *Low supply voltage will hamper high dynamic range*
- Increasing attention will have to be paid to interconnect at the technology, circuit, and architecture levels